

Lab 2 Attendance		
Name	2/21	2/28
Raul Muniz	RM	-
Brian Bowman	BB	-

Part 1

- I. **Problem:** Display a 4-bit binary-coded-decimal (BCD) on a 7-segment display.
- II. **Conceptual Design:** The rightmost four switches, SW[3:0] are used to input the BCD, and the rightmost 7-segment display, HEX0, will output the number. If a number greater than 9 is input, the output is blank.
- III. **Verilog Design:**

```

module bcd2leds (bcd, leds);
    input [3:0] bcd;
    output reg [6:0] leds;


    always @ (*) begin
        case (bcd)
            4'b0000 : leds = 7'b1000000; // 0
            4'b0001 : leds = 7'b1111001; // 1
            4'b0010 : leds = 7'b0100100; // 2
            4'b0011 : leds = 7'b0110000; // 3
            4'b0100 : leds = 7'b0011001; // 4
            4'b0101 : leds = 7'b0010010; // 5
            4'b0110 : leds = 7'b0000010; // 6
            4'b0111 : leds = 7'b1111000; // 7
            4'b1000 : leds = 7'b0000000; // 8
            4'b1001 : leds = 7'b0010000; // 9
            default : leds = 7'b1111111; // blank
        endcase
    end
endmodule

module lab2part1 (SW, HEX0);
    input [3:0] SW;
    output [6:0] HEX0;

    bcd2leds U0 (SW, HEX0);
endmodule

```

IV. Lab Procedure: Pictures

 


Troubleshooting: n/a

Conclusion: The lab was straightforward. The bcd2leds module is just like the module from lab 1 that displays the characters 'h', 'e', 'l', 'o', except this module displays numbers.

Part 2

- I. **Problem:** Use three instances of the module from part 1 to display a 3-digit BCD number on the three 7-segment displays HEX2-HEX0, with each digit being controlled by four switches.

II. Conceptual Design:

 

III. Verilog Design:


```

module lab2part2 (SW, HEX0, HEX1, HEX2);
    input [11:0] SW;
    output [6:0] HEX0, HEX1, HEX2;

    bcd2leds U0 (SW[3:0], HEX0);
    bcd2leds U1 (SW[7:4], HEX1);
    bcd2leds U2 (SW[11:8], HEX2);
endmodule

```

IV. Lab Procedure: Pictures

 

Troubleshooting: n/a

Conclusion: This part was straightforward, just consisting of three instances of part 1.

Part 3

- I. **Problem:** Compute the sum of two single-digit numbers, and display the input and output digits over four 7-segment displays.
- II. **Conceptual Design:** The eight rightmost switches are used to input the two digits to be summed. These inputs are fed to the bcdadd1 module which computes the 2-digit sum, and are also displayed on HEX4 and HEX6 using the bcd2leds module. The sum is displayed on the two rightmost 7-segment displays using the bcd2leds module.
- III. **Verilog Design**

```

module bcdadd1 (a0, b0, s0, s1);
    input [3:0] a0, b0;
    output [3:0] s0;
    output s1;

    assign s0 = (a0 + b0) % 10;
    assign s1 = (a0 + b0) / 10;
endmodule

module lab2part3 (SW, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, HEX6, HEX7);
    input [7:0] SW;
    output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, HEX6, HEX7;
    wire s1; // tens sum digit
    wire [3:0] s0; // ones sum digit

    // blank unused 7-segment displays
    assign HEX2 = 7'b1111111;
    assign HEX3 = 7'b1111111;
    assign HEX5 = 7'b1111111;
    assign HEX7 = 7'b1111111;


    // display input
    bcd2leds U0 (SW[3:0], HEX4);
    bcd2leds U1 (SW[7:4], HEX6);

    // display sum
    bcd2leds U2 (s0, HEX0);
    bcd2leds U3 (s1, HEX1);

    // calculate sum
    bcdadd1 U4 (SW[3:0], SW[7:4], s0, s1);
endmodule

```


IV. Lab Procedure: Pictures

 

Troubleshooting: n/a

Conclusion: We managed to successfully execute the correct output by assigning accordingly the correct number of inputs and outputs which were 3 as in the parts before. Then s0 will be set to the number of the input of LEDS mod 10. S1 will be a direct integer division of the input of LEDS by 10. Next the module "lab2part3" assigned each digit accordingly with blanks and corresponding switches with LEDS.

Part 4

- I. **Problem:** Compute the sum of two two-digit numbers, and display the input and output digits over seven 7-segment displays.
- II. **Conceptual Design:** The two numbers to be added are input using SW[15:0]. The inputs are visualized on HEX4-7. The result of the addition is displayed on HEX0-2. HEX3, which isn't used, is turned off to make reading the inputs and outputs easier.
- III. **Verilog Design:**

```
module bcdadd1fa (a0, b0, c_in, s0, c_out);
    input [3:0] a0, b0;
    input c_in;
    output [3:0] s0;
    output c_out;

    assign s0 = (a0 + b0 + c_in) % 10;
    assign c_out = (a0 + b0 + c_in) / 10;
endmodule

module lab2part4 (SW, HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, HEX6, HEX7);
    input [15:0] SW;
    output [6:0] HEX0, HEX1, HEX2, HEX3, HEX4, HEX5, HEX6, HEX7;
    wire c0, c1; // carries
    wire [3:0] s0, s1; // ones and tens digits

    // blank unused 7-segment display
    assign HEX3 = 7'b1111111;

    // display input
    bcd2leds U0 (SW[3:0], HEX4);
    bcd2leds U1 (SW[7:4], HEX5);
    bcd2leds U2 (SW[11:8], HEX6);
    bcd2leds U3 (SW[15:12], HEX7);


    // display sum
    bcd2leds U4 (s0, HEX0);
    bcd2leds U5 (s1, HEX1);
    bcd2leds U6 (c1, HEX2);

    // calculate sum
    bcdadd1fa U7 (SW[3:0], SW[11:8], 0, s0, c0);
    bcdadd1fa U8 (SW[7:4], SW[15:12], c0, s1, c1);
```

endmodule

IV. Lab Procedure:

Pictures:

 

Troubleshooting: n/a

Conclusion: In conclusion, we managed to successfully execute the correct output by assigning accordingly the correct number of inputs and outputs which were 3 as in the parts before. Then s_0 will be set to the number of the input of LEDs mod 10. s_1 will be a direct integer division of the input of LEDs by 10. Next the module "lab2part4" assigned each digit accordingly with blanks and corresponding switches with LEDs.